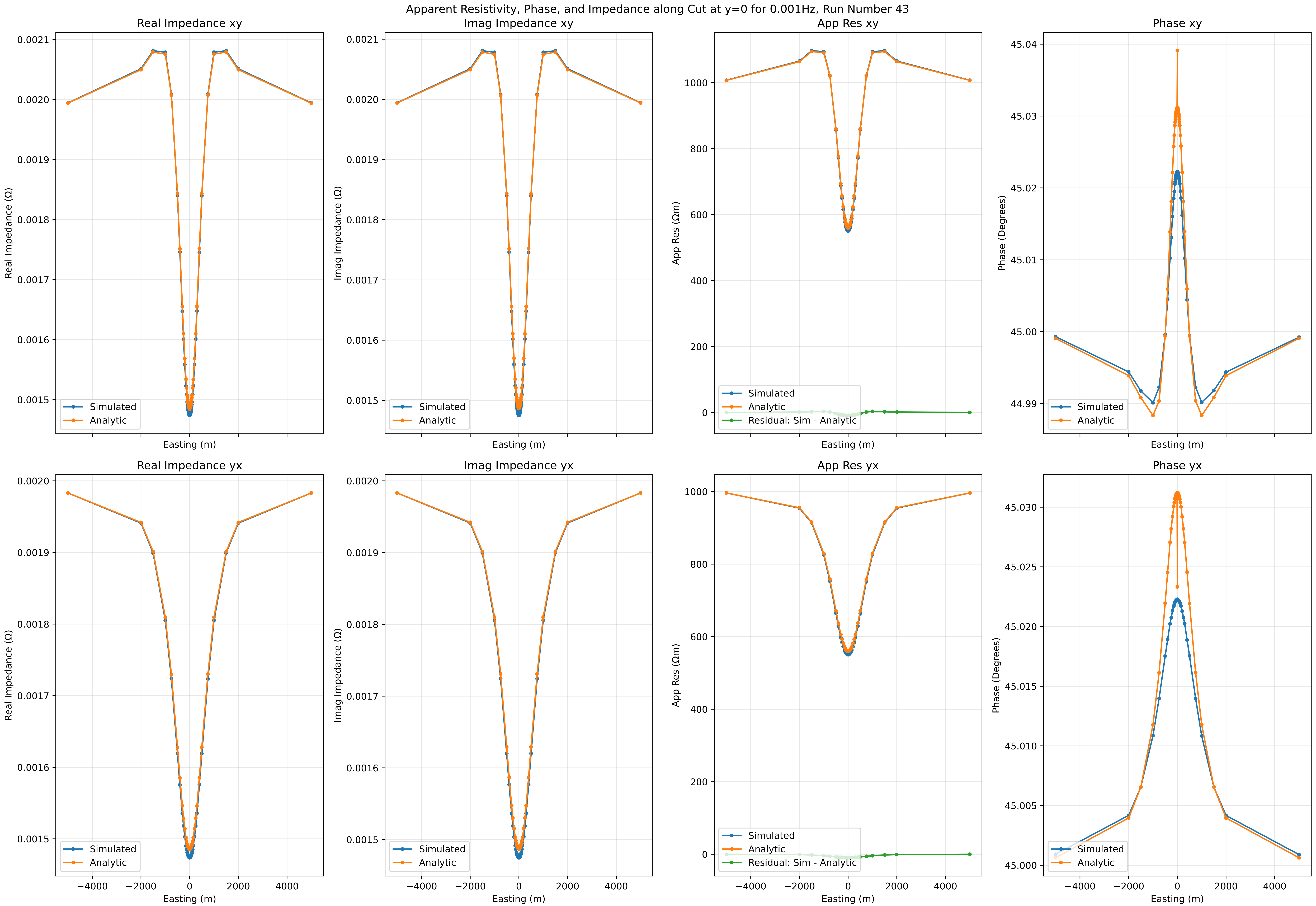
Apparent Resistivity, Phase, and Impedance along Cut at y=0 for 0.001Hz, Run Number 43
Real Impedance xy
Imag Impedance xy
App Res xy
Phase xy
Real Impedance yx
Imag Impedance yx
App Res yx
Phase yx
Real Impedance (Ω)
Imag Impedance (Ω)
App Res (Ωm)
Phase (Degrees)
Easting (m)
Simulated
Analytic
Residual: Sim - Analytic

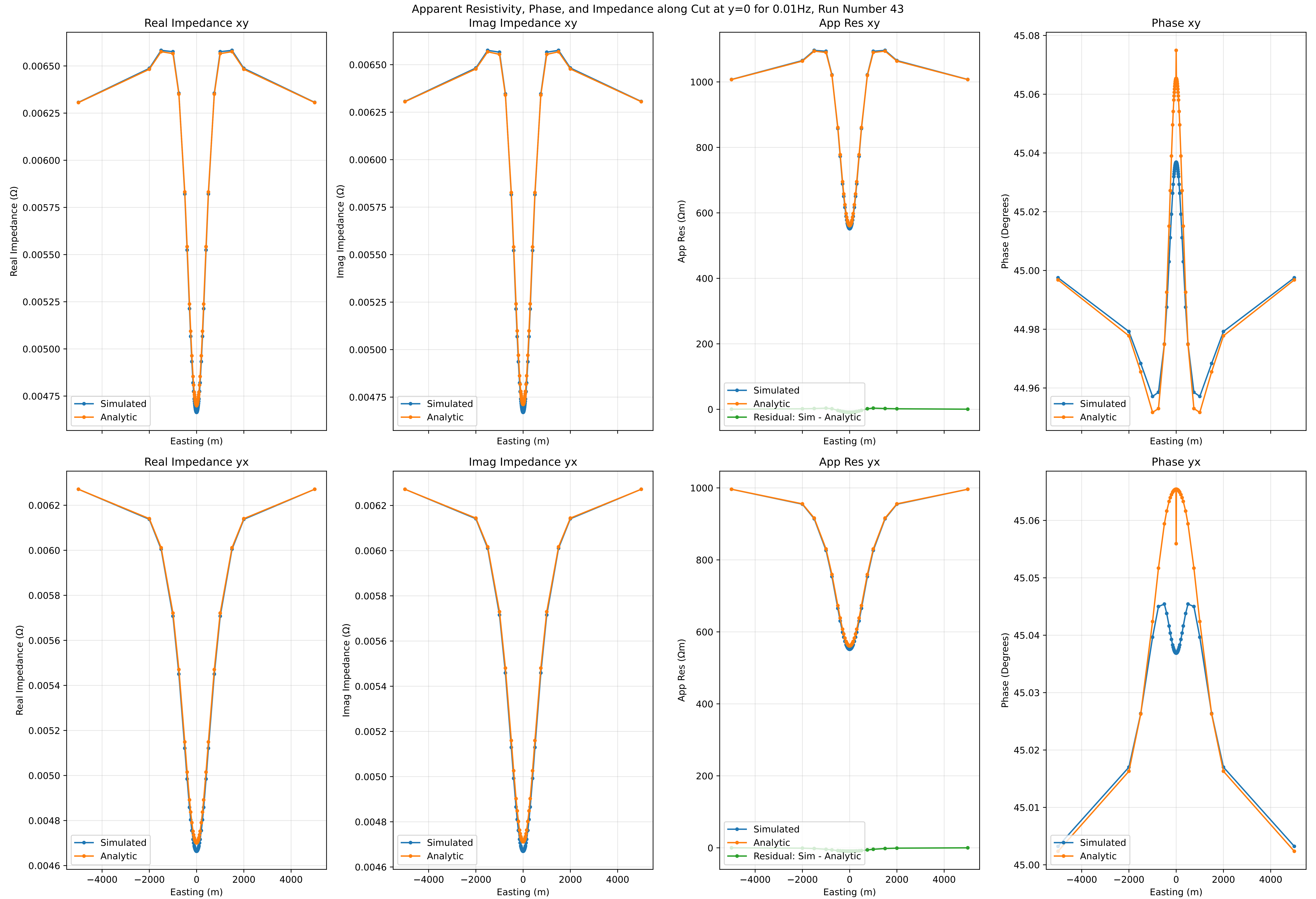

Apparent Resistivity, Phase, and Impedance along Cut at y=0 for 0.01Hz, Run Number 43
Real Impedance xy
Imag Impedance xy
App Res xy
Phase xy
Real Impedance yx
Imag Impedance yx
App Res yx
Phase yx
Real Impedance (Ω)
Imag Impedance (Ω)
App Res (Ωm)
Phase (Degrees)
Easting (m)
Simulated
Analytic
Residual: Sim - Analytic

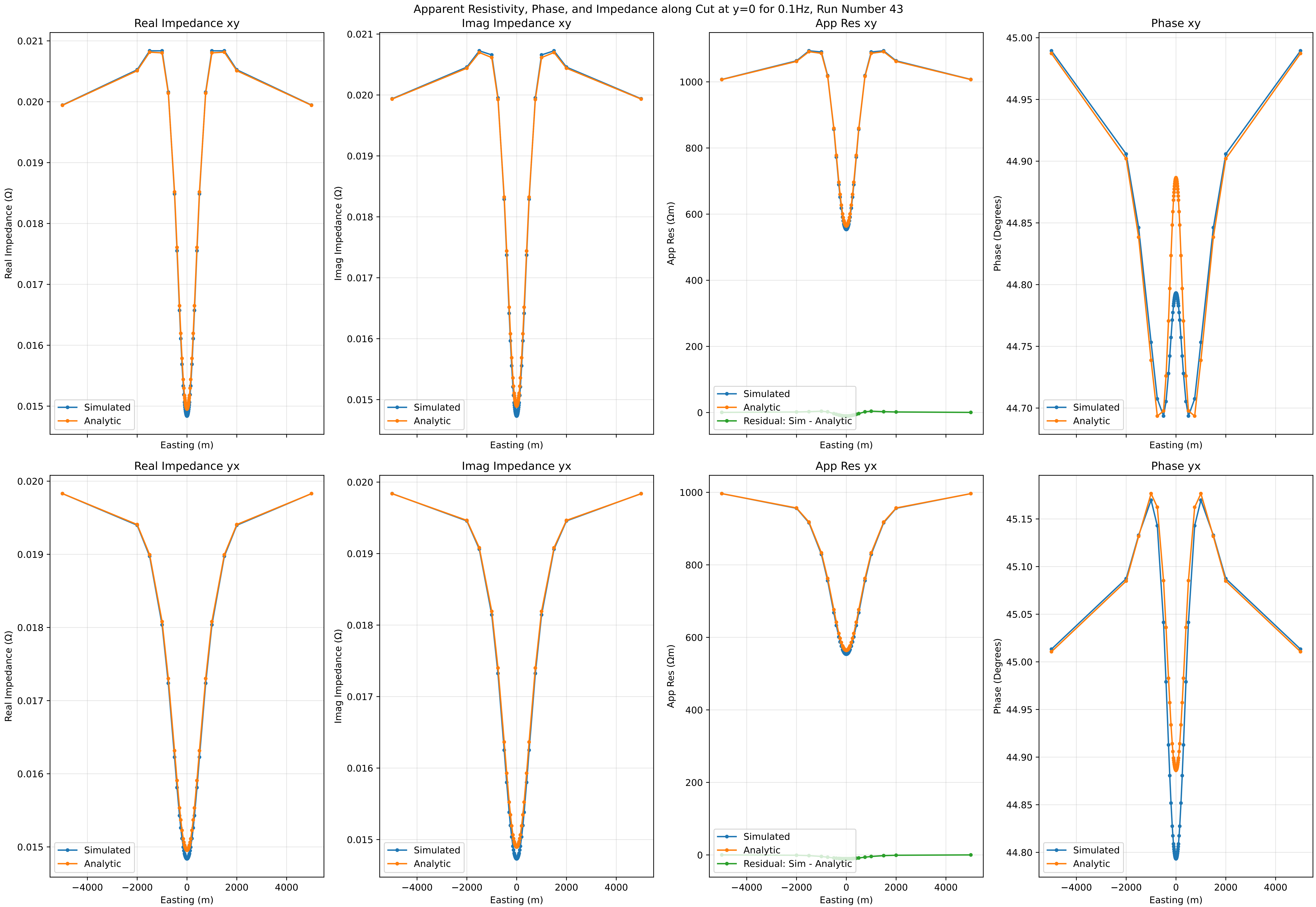

Apparent Resistivity, Phase, and Impedance along Cut at y=0 for 0.1Hz, Run Number 43
Real Impedance xy
Imag Impedance xy
App Res xy
Phase xy
Real Impedance yx
Imag Impedance yx
App Res yx
Phase yx
Real Impedance (Ω)
Imag Impedance (Ω)
App Res (Ωm)
Phase (Degrees)
Easting (m)
Simulated
Analytic
Residual: Sim - Analytic

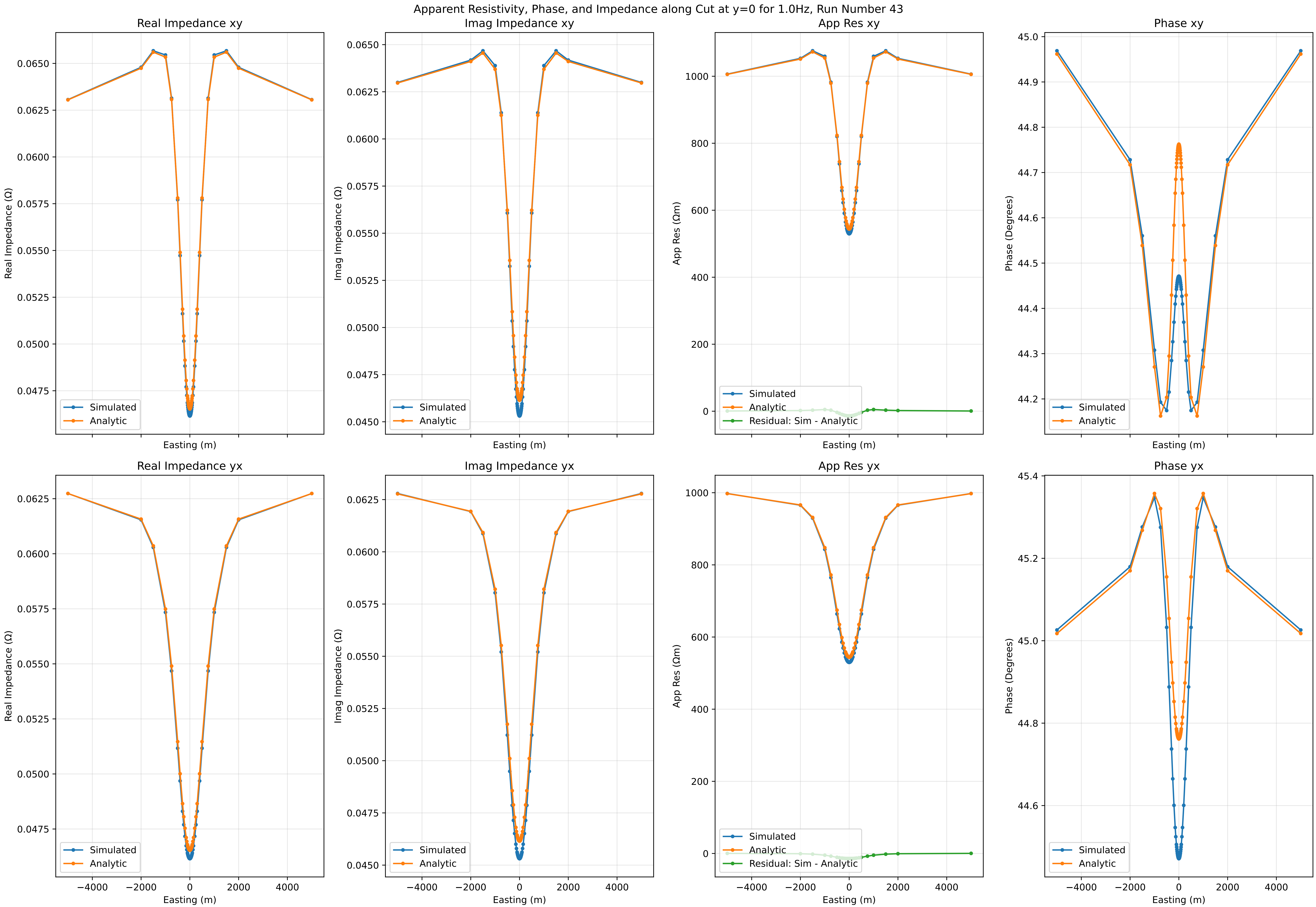

Apparent Resistivity, Phase, and Impedance along Cut at y=0 for 1.0Hz, Run Number 43
Real Impedance xy
Imag Impedance xy
App Res xy
Phase xy
Real Impedance yx
Imag Impedance yx
App Res yx
Phase yx
Real Impedance (Ω)
Imag Impedance (Ω)
App Res (Ωm)
Phase (Degrees)
Easting (m)
Simulated
Analytic
Residual: Sim - Analytic

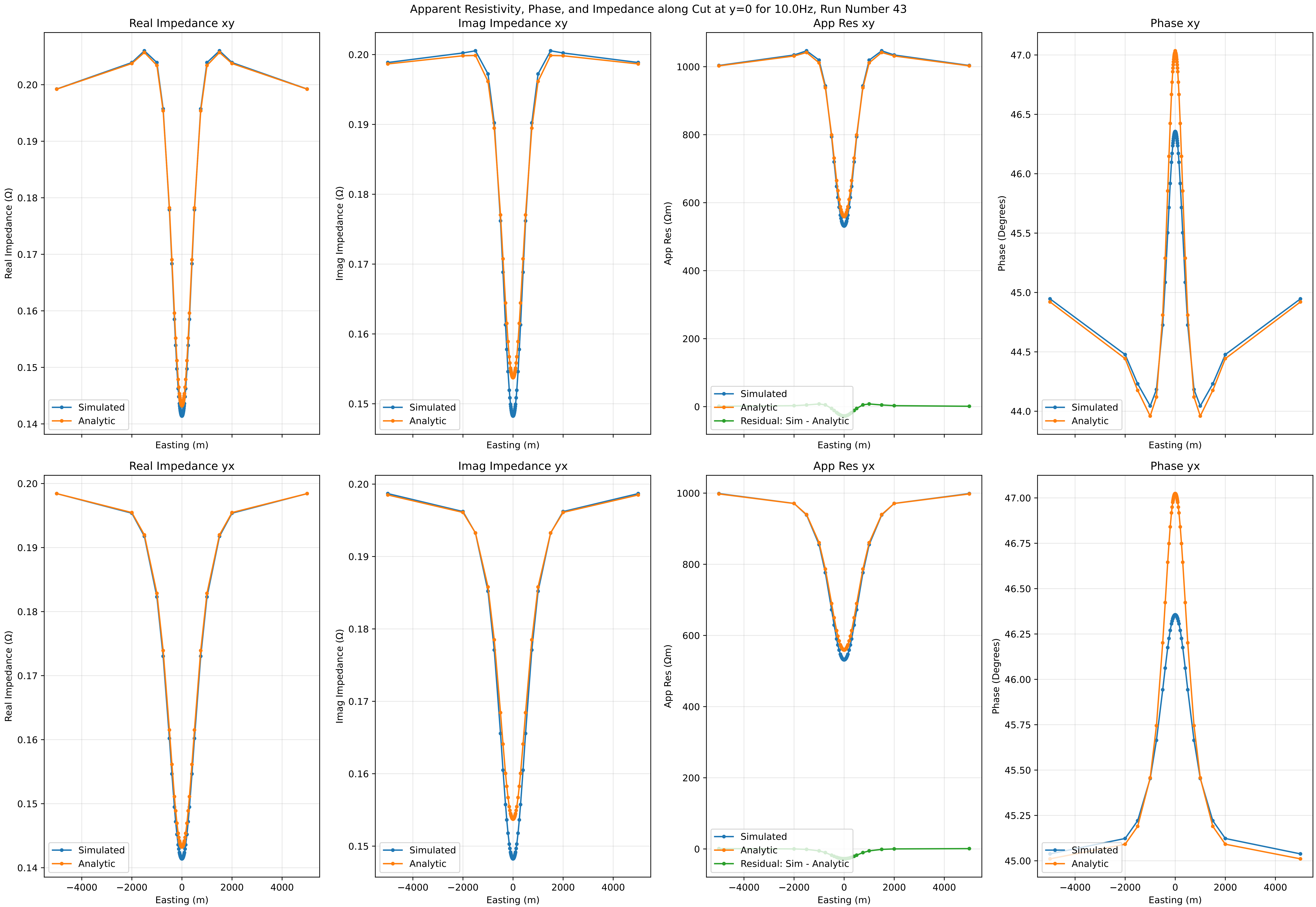
Apparent Resistivity, Phase, and Impedance along Cut at y=0 for 10.0Hz, Run Number 43
Real Impedance xy
Real Impedance (Ω)
Easting (m)
Simulated
Analytic
Imag Impedance xy
Imag Impedance (Ω)
Easting (m)
Simulated
Analytic
App Res xy
App Res (Ωm)
Easting (m)
Simulated
Analytic
Residual: Sim - Analytic
Phase xy
Phase (Degrees)
Easting (m)
Simulated
Analytic
Real Impedance yx
Real Impedance (Ω)
Easting (m)
Simulated
Analytic
Imag Impedance yx
Imag Impedance (Ω)
Easting (m)
Simulated
Analytic
App Res yx
App Res (Ωm)
Easting (m)
Simulated
Analytic
Residual: Sim - Analytic
Phase yx
Phase (Degrees)
Easting (m)
Simulated
Analytic

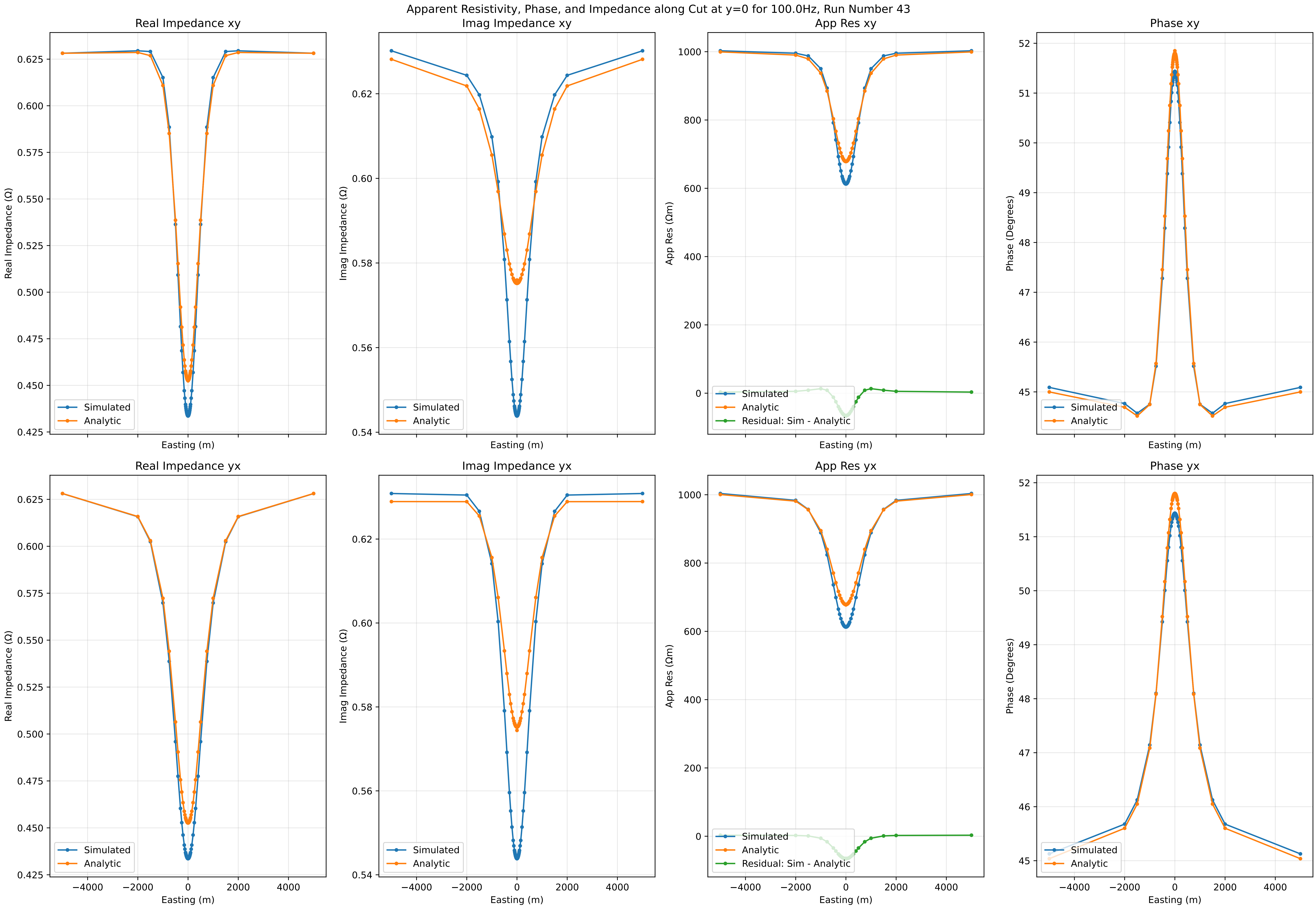

Apparent Resistivity, Phase, and Impedance along Cut at y=0 for 100.0Hz, Run Number 43
Real Impedance xy
Imag Impedance xy
App Res xy
Phase xy
Real Impedance yx
Imag Impedance yx
App Res yx
Phase yx
Real Impedance (Ω)
Imag Impedance (Ω)
App Res (Ωm)
Phase (Degrees)
Easting (m)
Simulated
Analytic
Residual: Sim - Analytic

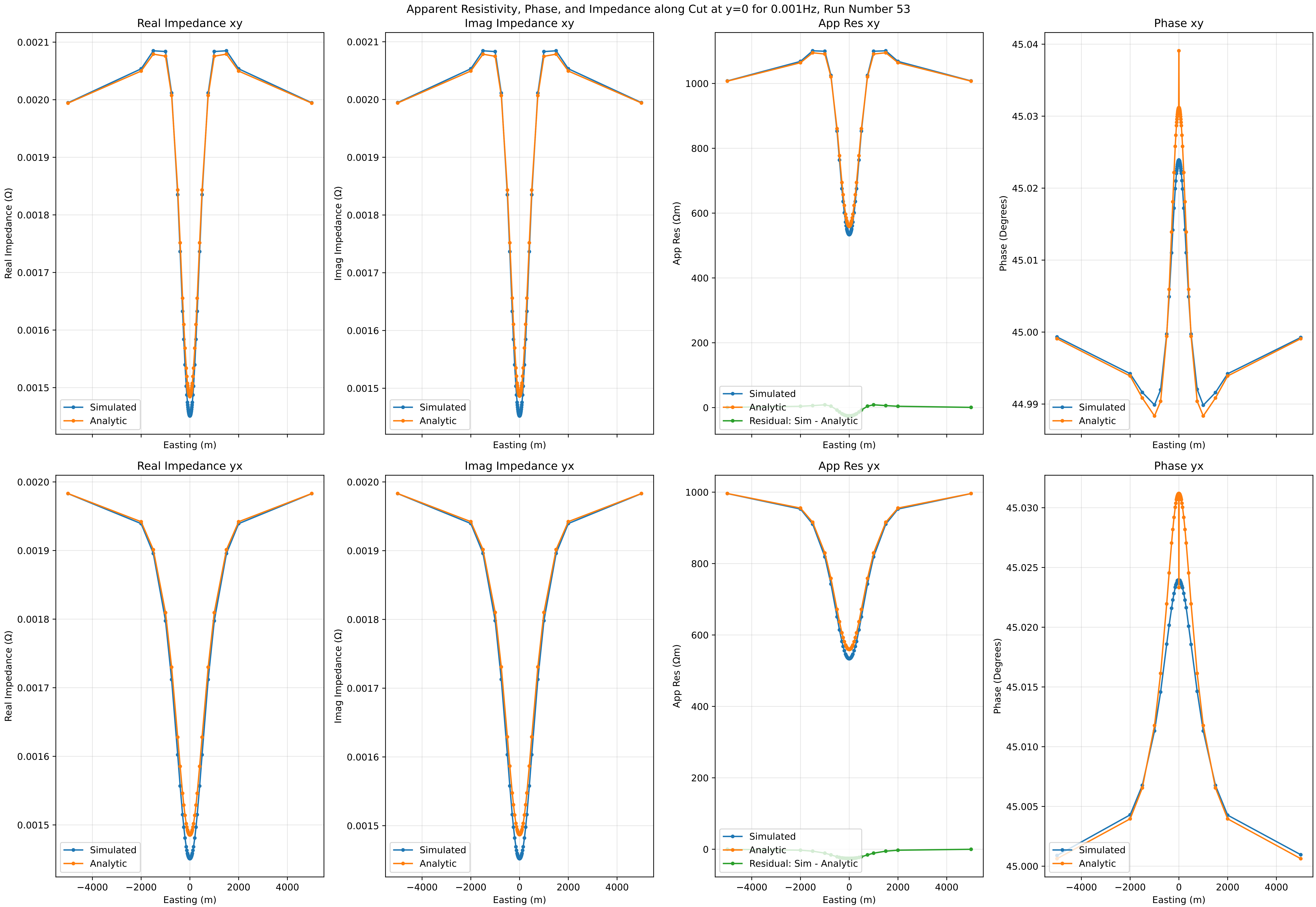
Apparent Resistivity, Phase, and Impedance along Cut at y=0 for 0.001Hz, Run Number 53
Real Impedance xy
Imag Impedance xy
App Res xy
Phase xy
Real Impedance yx
Imag Impedance yx
App Res yx
Phase yx
Real Impedance (Ω)
Imag Impedance (Ω)
App Res (Ωm)
Phase (Degrees)
Easting (m)
Simulated
Analytic
Residual: Sim - Analytic

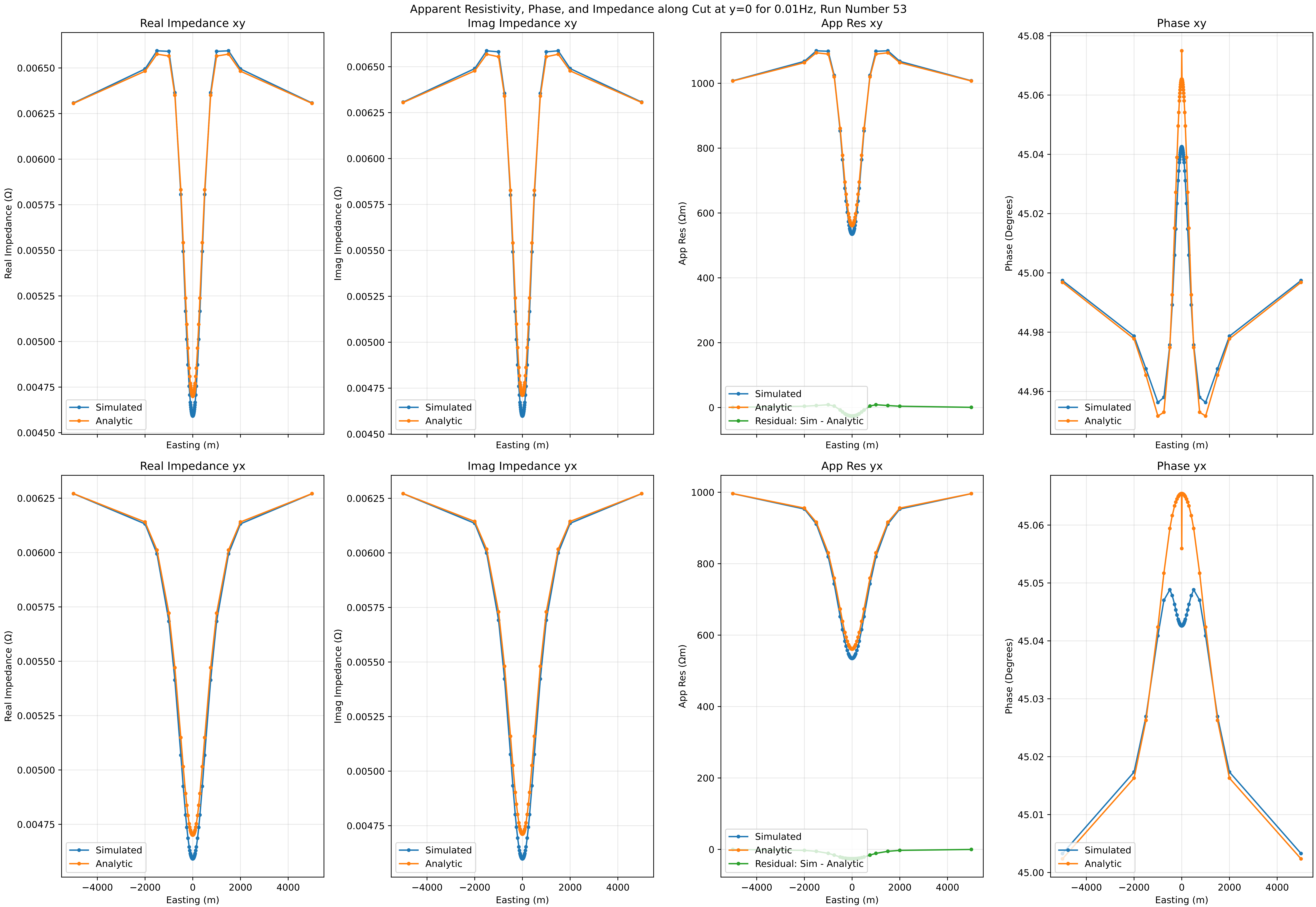

Apparent Resistivity, Phase, and Impedance along Cut at y=0 for 0.01Hz, Run Number 53
Real Impedance xy
Imag Impedance xy
App Res xy
Phase xy
Real Impedance yx
Imag Impedance yx
App Res yx
Phase yx
Real Impedance (Ω)
Imag Impedance (Ω)
App Res (Ωm)
Phase (Degrees)
Easting (m)
Simulated
Analytic
Residual: Sim - Analytic

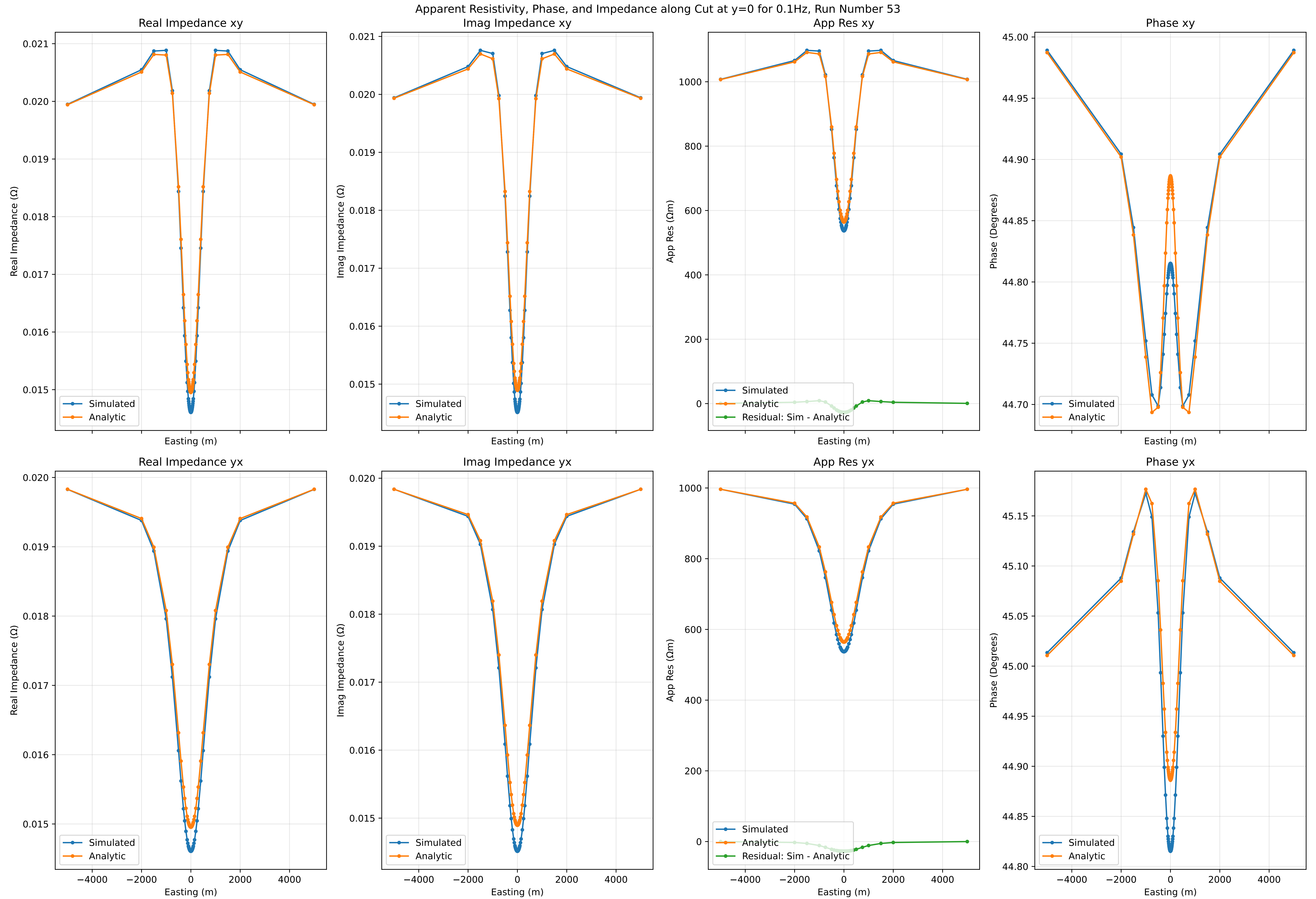

Apparent Resistivity, Phase, and Impedance along Cut at y=0 for 0.1Hz, Run Number 53
Real Impedance xy
Imag Impedance xy
App Res xy
Phase xy
Real Impedance yx
Imag Impedance yx
App Res yx
Phase yx
Real Impedance (Ω)
Imag Impedance (Ω)
App Res (Ωm)
Phase (Degrees)
Easting (m)
Simulated
Analytic
Residual: Sim - Analytic

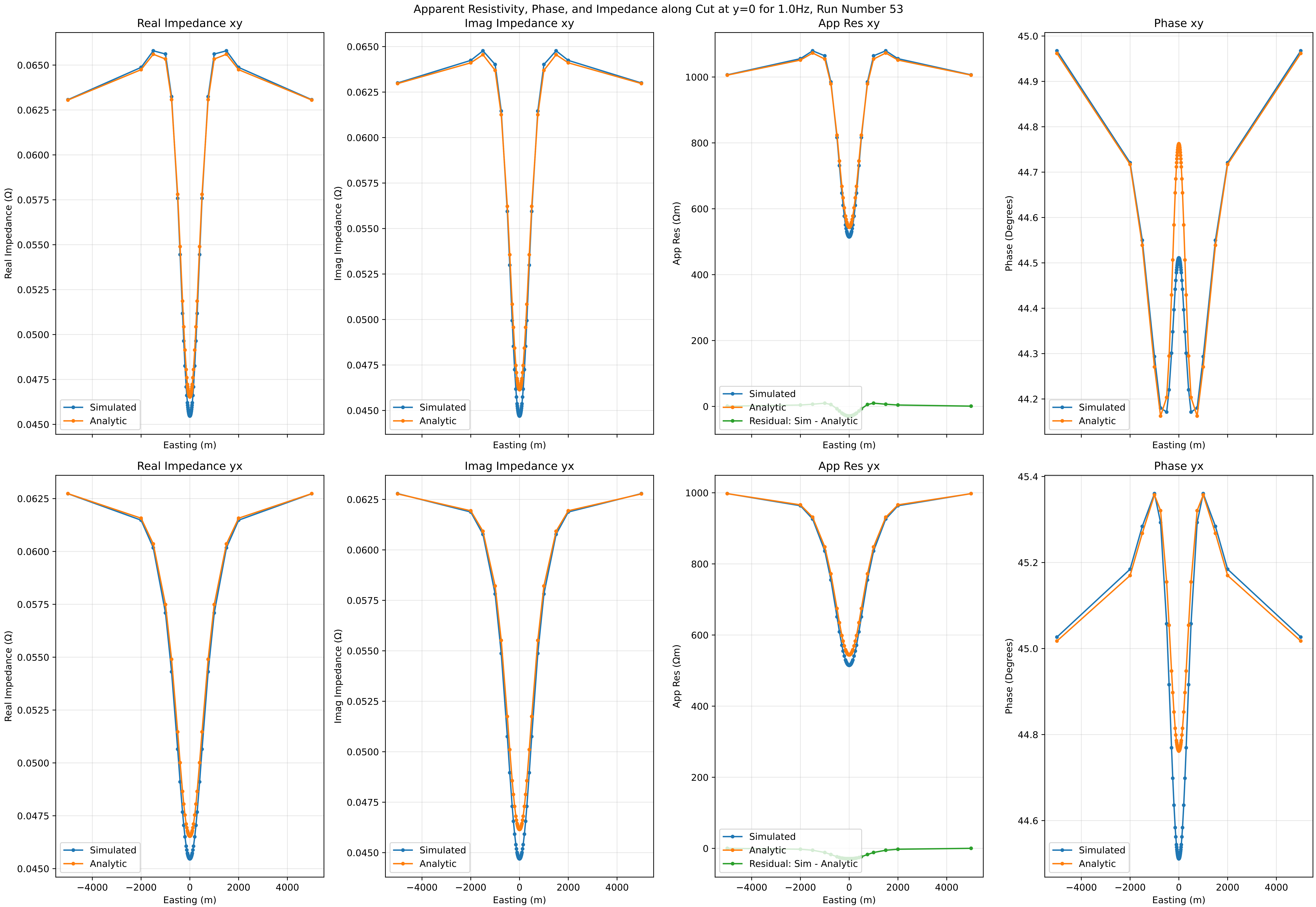

Apparent Resistivity, Phase, and Impedance along Cut at y=0 for 1.0Hz, Run Number 53
Real Impedance xy
Imag Impedance xy
App Res xy
Phase xy
Real Impedance yx
Imag Impedance yx
App Res yx
Phase yx
Real Impedance (Ω)
Imag Impedance (Ω)
App Res (Ωm)
Phase (Degrees)
Easting (m)
Simulated
Analytic
Residual: Sim - Analytic

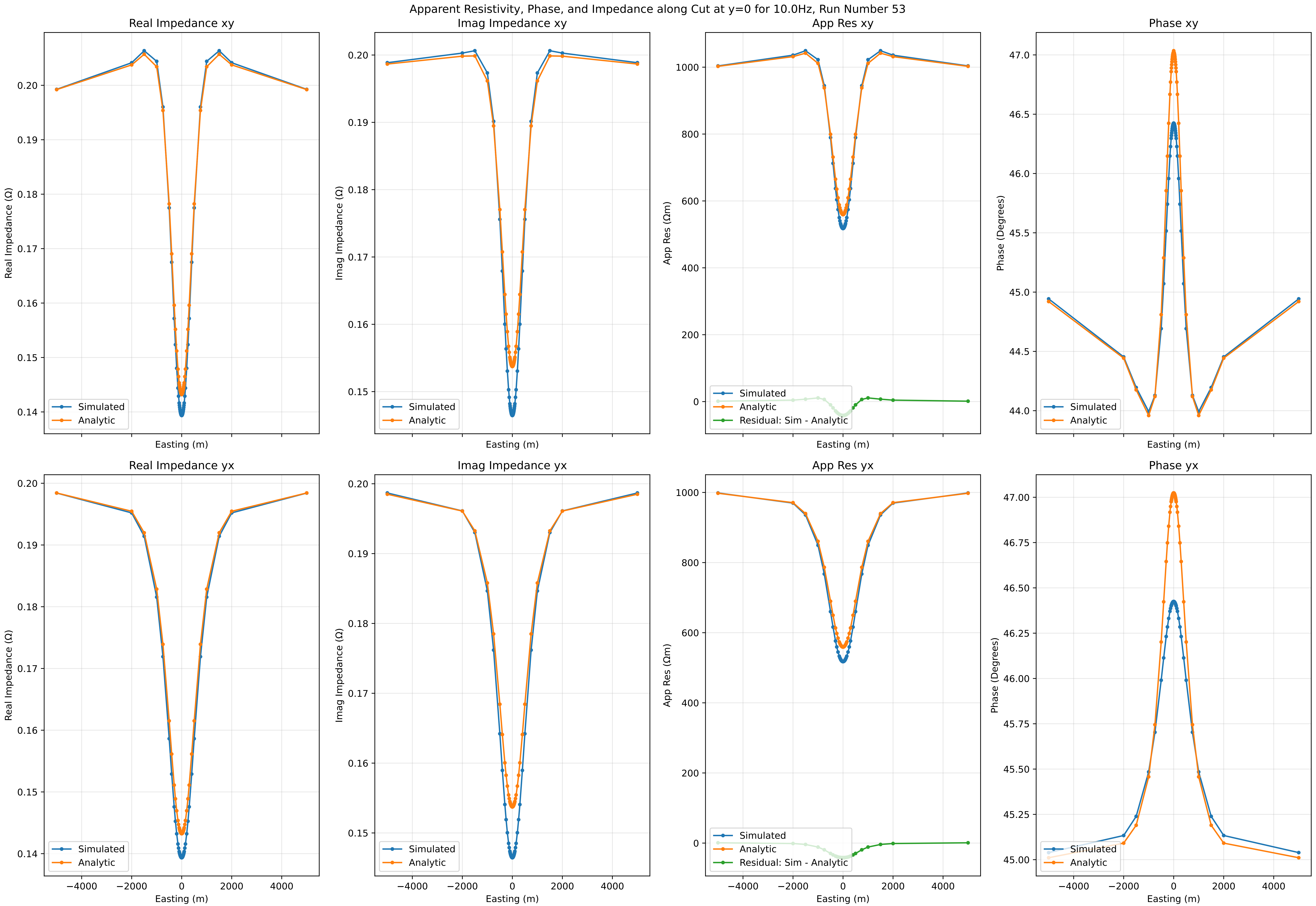
Apparent Resistivity, Phase, and Impedance along Cut at y=0 for 10.0Hz, Run Number 53
Real Impedance xy
Imag Impedance xy
App Res xy
Phase xy
Real Impedance yx
Imag Impedance yx
App Res yx
Phase yx
Real Impedance (Ω)
Imag Impedance (Ω)
App Res (Ωm)
Phase (Degrees)
Easting (m)
Simulated
Analytic
Residual: Sim - Analytic

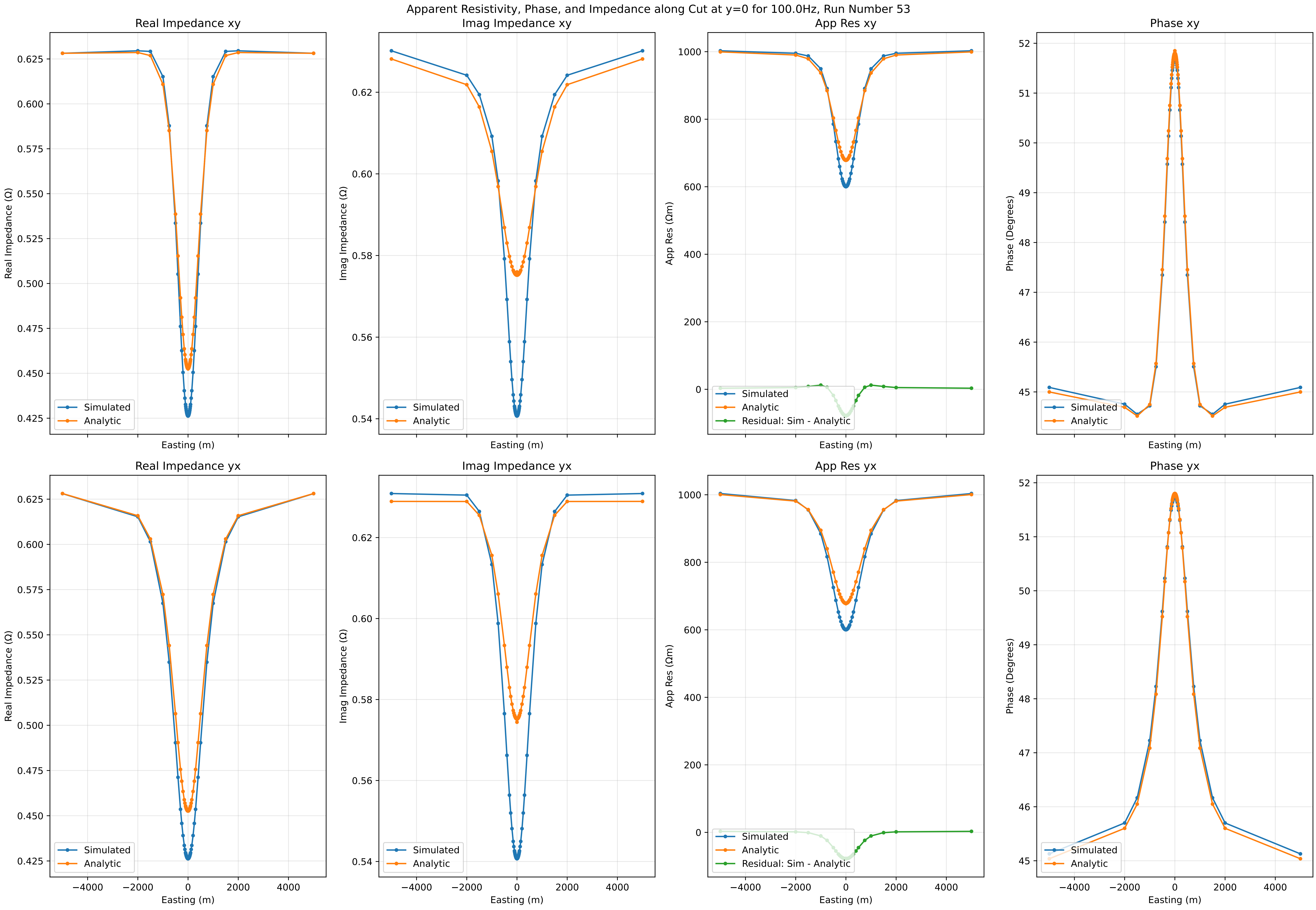
Apparent Resistivity, Phase, and Impedance along Cut at y=0 for 100.0Hz, Run Number 53
Real Impedance xy
Imag Impedance xy
App Res xy
Phase xy
Real Impedance yx
Imag Impedance yx
App Res yx
Phase yx
Real Impedance (Ω)
Imag Impedance (Ω)
App Res (Ωm)
Phase (Degrees)
Easting (m)
Simulated
Analytic
Residual: Sim - Analytic

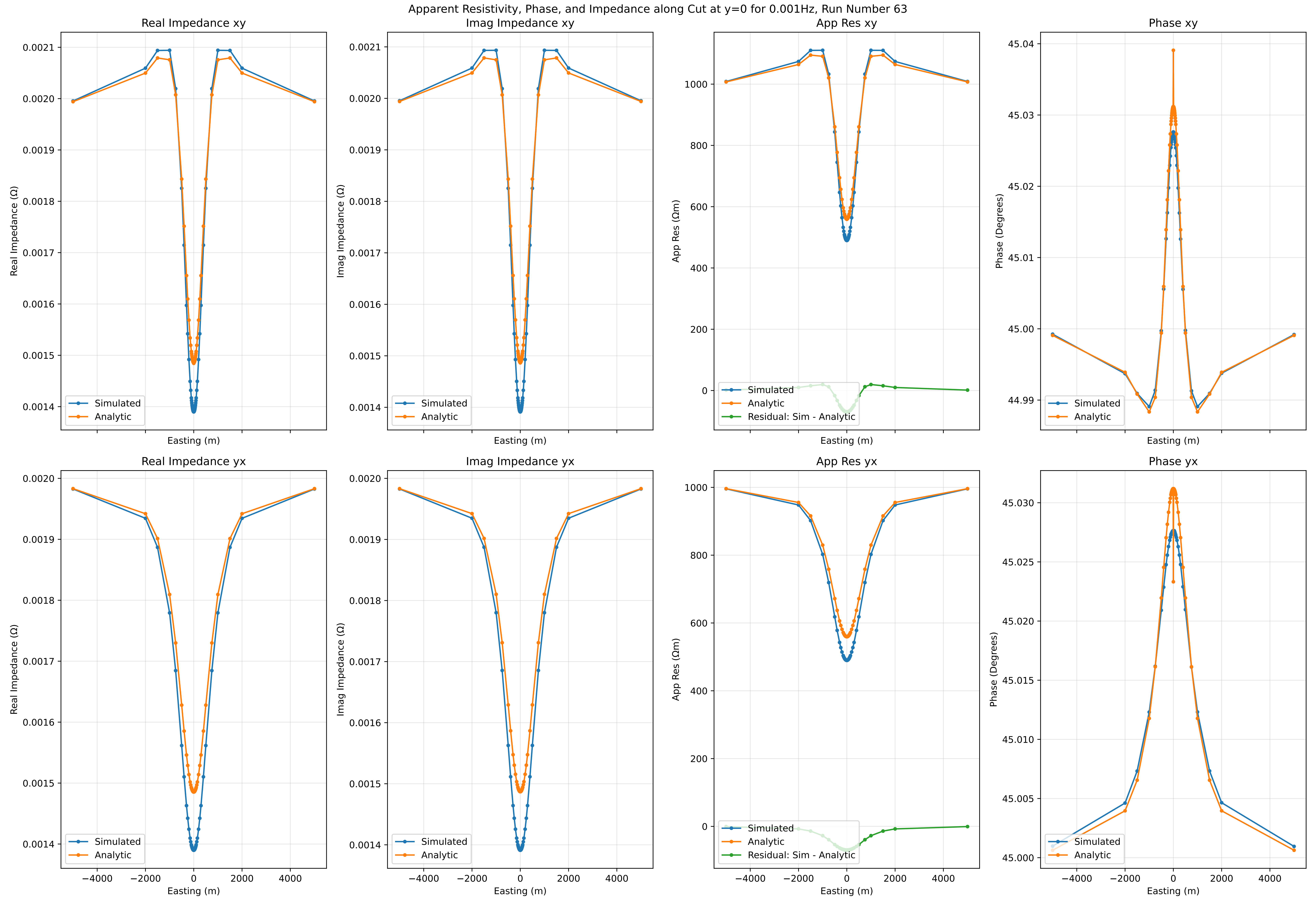
Apparent Resistivity, Phase, and Impedance along Cut at y=0 for 0.001Hz, Run Number 63
Real Impedance xy
Imag Impedance xy
App Res xy
Phase xy
Real Impedance yx
Imag Impedance yx
App Res yx
Phase yx
Real Impedance (Ω)
Imag Impedance (Ω)
App Res (Ωm)
Phase (Degrees)
Easting (m)
Simulated
Analytic
Residual: Sim - Analytic

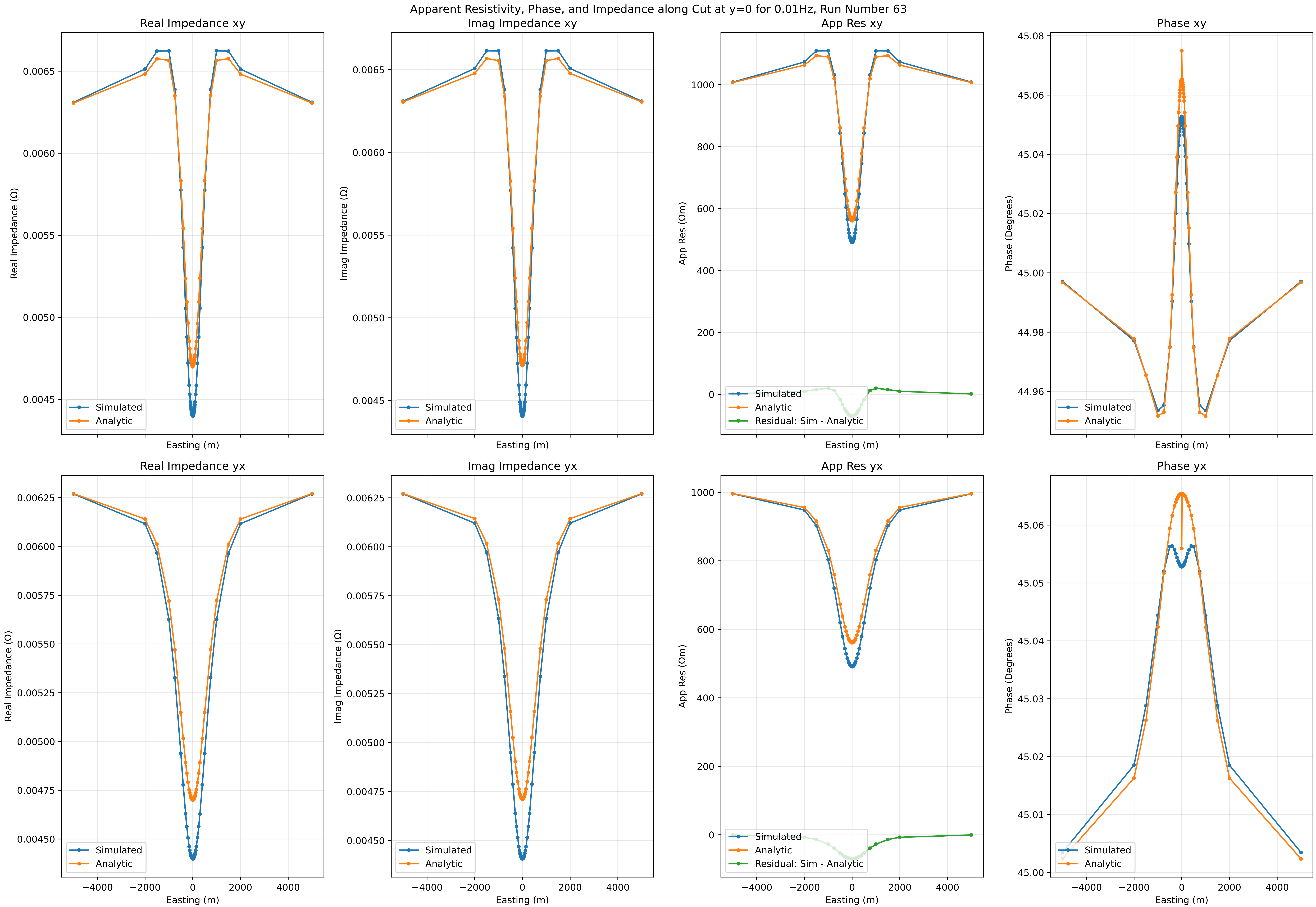

Apparent Resistivity, Phase, and Impedance along Cut at y=0 for 0.01Hz, Run Number 63
Real Impedance xy
Imag Impedance xy
App Res xy
Phase xy
Real Impedance yx
Imag Impedance yx
App Res yx
Phase yx
Real Impedance (Ω)
Imag Impedance (Ω)
App Res (Ωm)
Phase (Degrees)
Easting (m)
Simulated
Analytic
Residual: Sim - Analytic

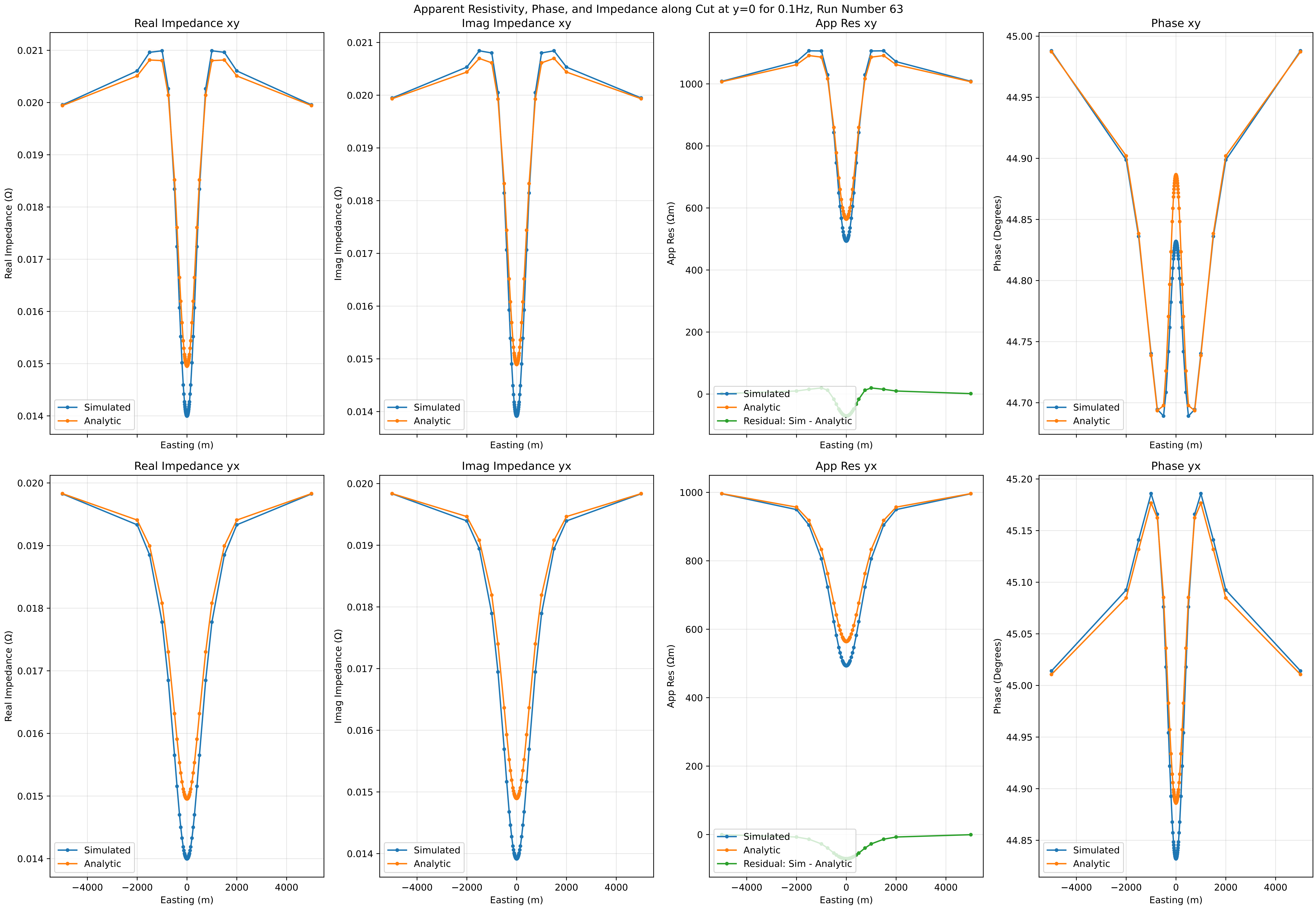
Apparent Resistivity, Phase, and Impedance along Cut at y=0 for 0.1Hz, Run Number 63
Real Impedance xy
Imag Impedance xy
App Res xy
Phase xy
Real Impedance yx
Imag Impedance yx
App Res yx
Phase yx
Real Impedance (Ω)
Imag Impedance (Ω)
App Res (Ωm)
Phase (Degrees)
Easting (m)
Simulated
Analytic
Residual: Sim - Analytic

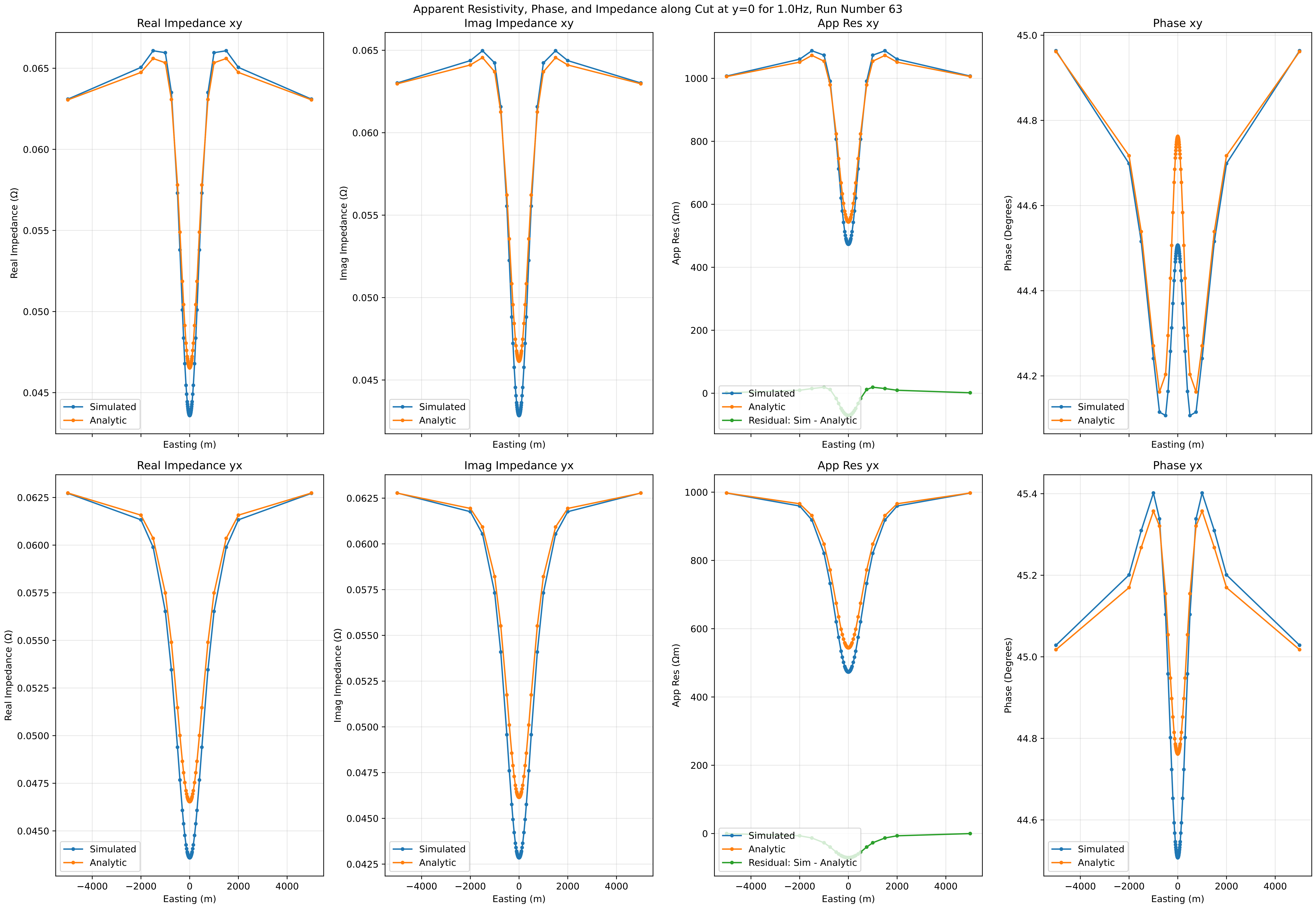

Apparent Resistivity, Phase, and Impedance along Cut at y=0 for 1.0Hz, Run Number 63
Real Impedance xy
Imag Impedance xy
App Res xy
Phase xy
Real Impedance yx
Imag Impedance yx
App Res yx
Phase yx
Real Impedance (Ω)
Imag Impedance (Ω)
App Res (Ωm)
Phase (Degrees)
Easting (m)
Simulated
Analytic
Residual: Sim - Analytic

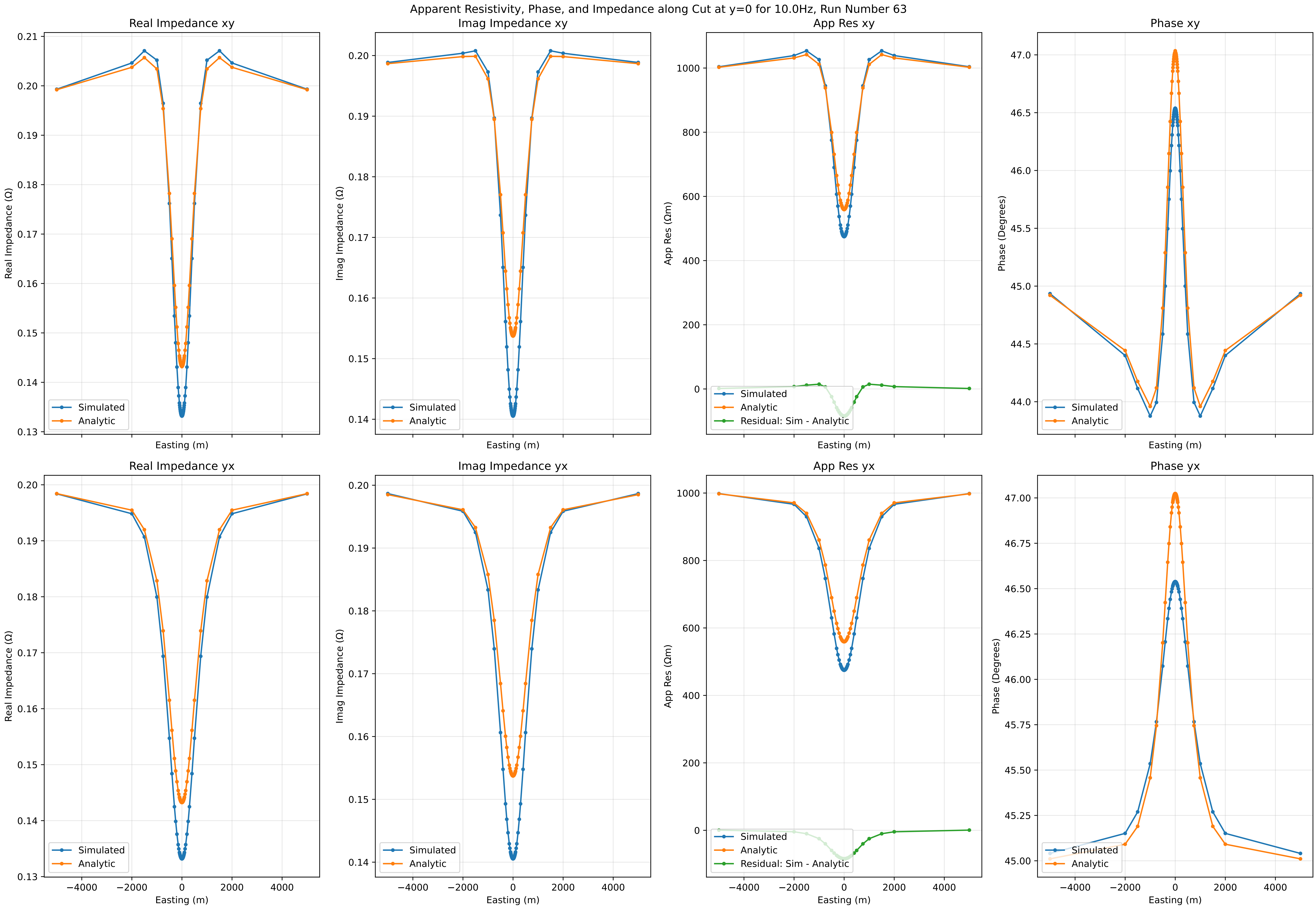
Apparent Resistivity, Phase, and Impedance along Cut at y=0 for 10.0Hz, Run Number 63
Real Impedance xy
Imag Impedance xy
App Res xy
Phase xy
Real Impedance yx
Imag Impedance yx
App Res yx
Phase yx
Real Impedance (Ω)
Imag Impedance (Ω)
App Res (Ωm)
Phase (Degrees)
Easting (m)
Simulated
Analytic
Residual: Sim - Analytic

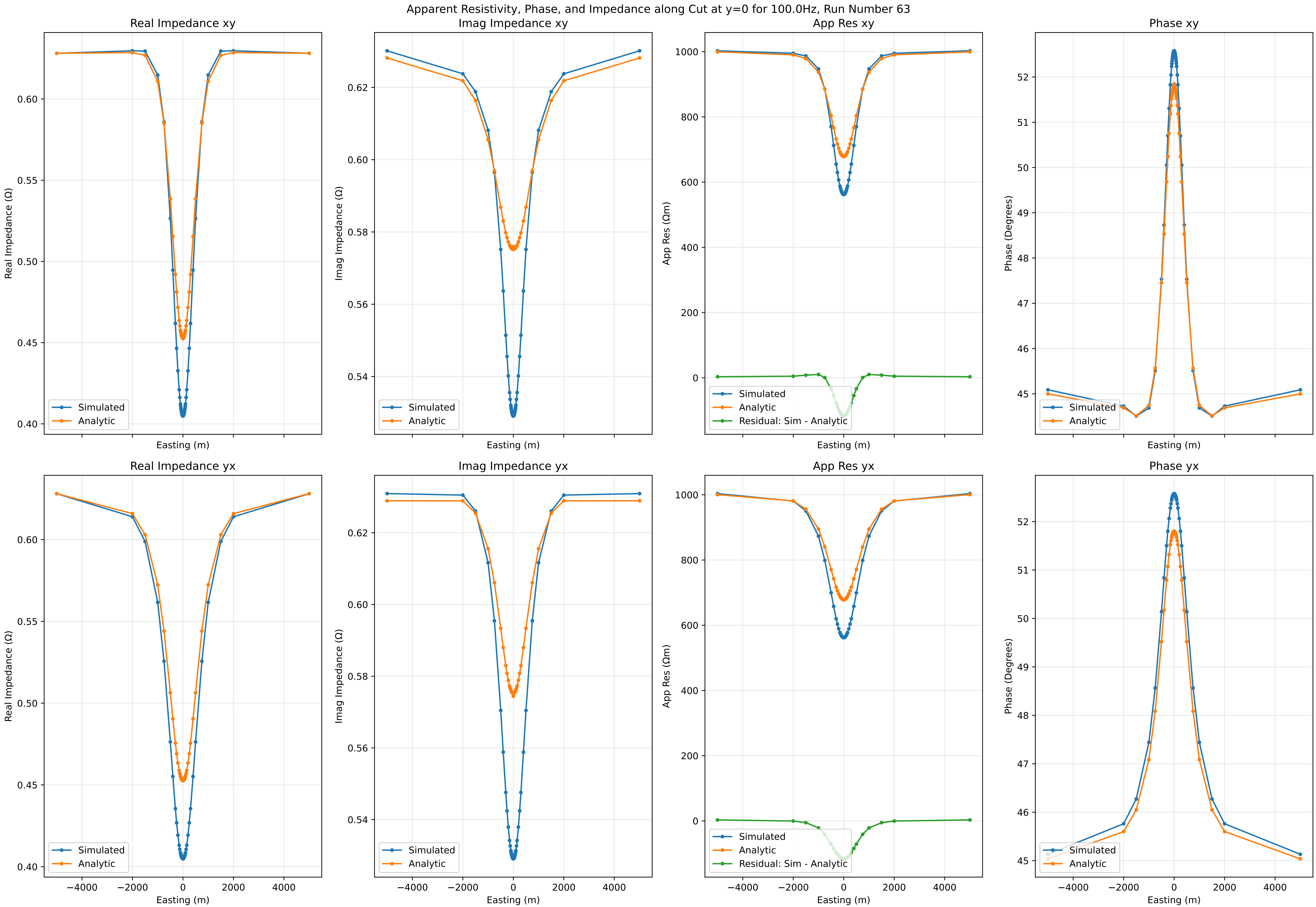

Apparent Resistivity, Phase, and Impedance along Cut at y=0 for 100.0Hz, Run Number 63
Real Impedance xy
Imag Impedance xy
App Res xy
Phase xy
Real Impedance yx
Imag Impedance yx
App Res yx
Phase yx
Real Impedance (Ω)
Imag Impedance (Ω)
App Res (Ωm)
Phase (Degrees)
Easting (m)
Simulated
Analytic
Residual: Sim - Analytic

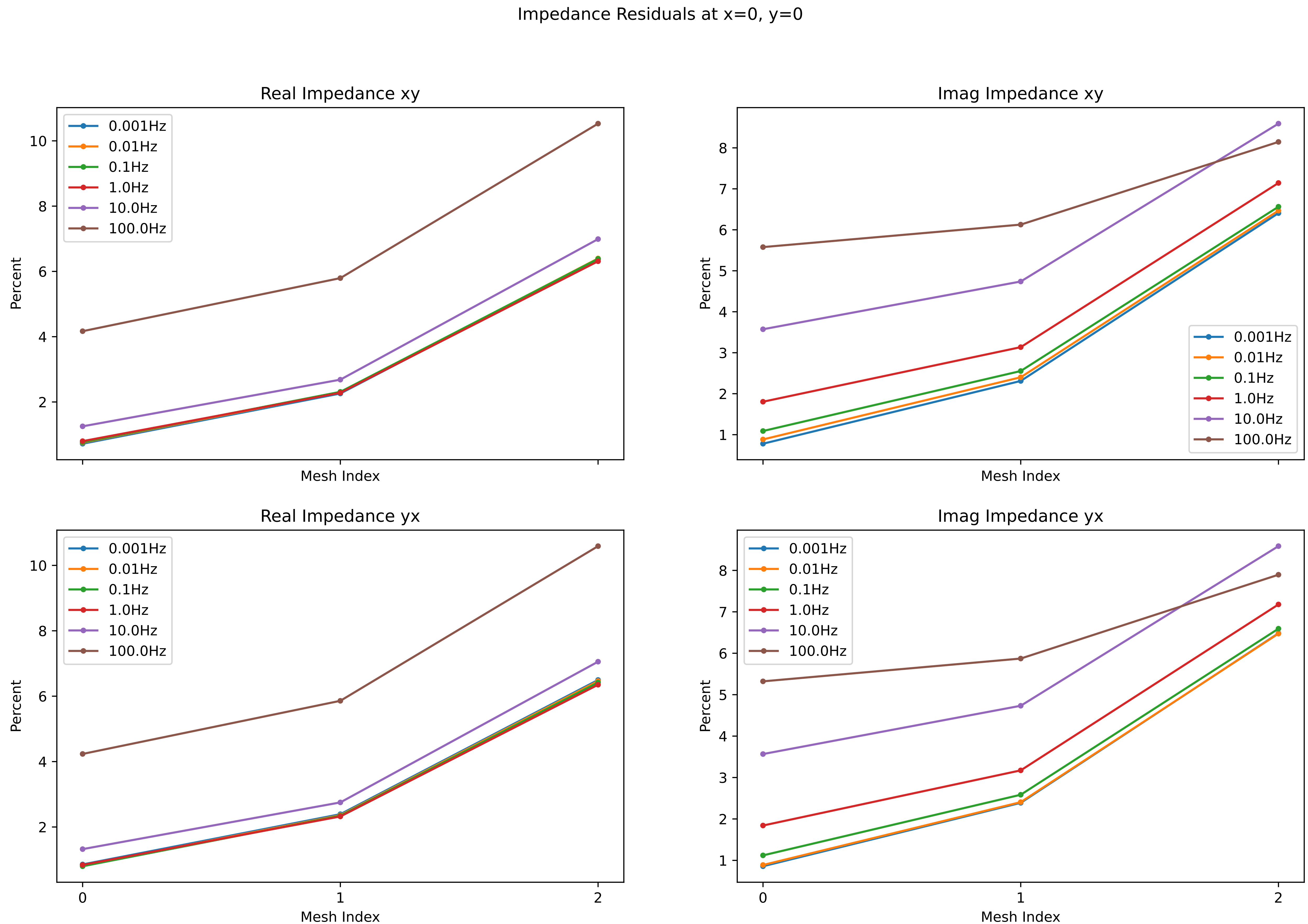
Impedance Residuals at x=0, y=0
Real Impedance xy
Imag Impedance xy
Real Impedance yx
Imag Impedance yx
0.001Hz
0.01Hz
0.1Hz
1.0Hz
10.0Hz
100.0Hz
Percent
Mesh Index
0
1
2
2
4
6
8
10
1
3
5
7

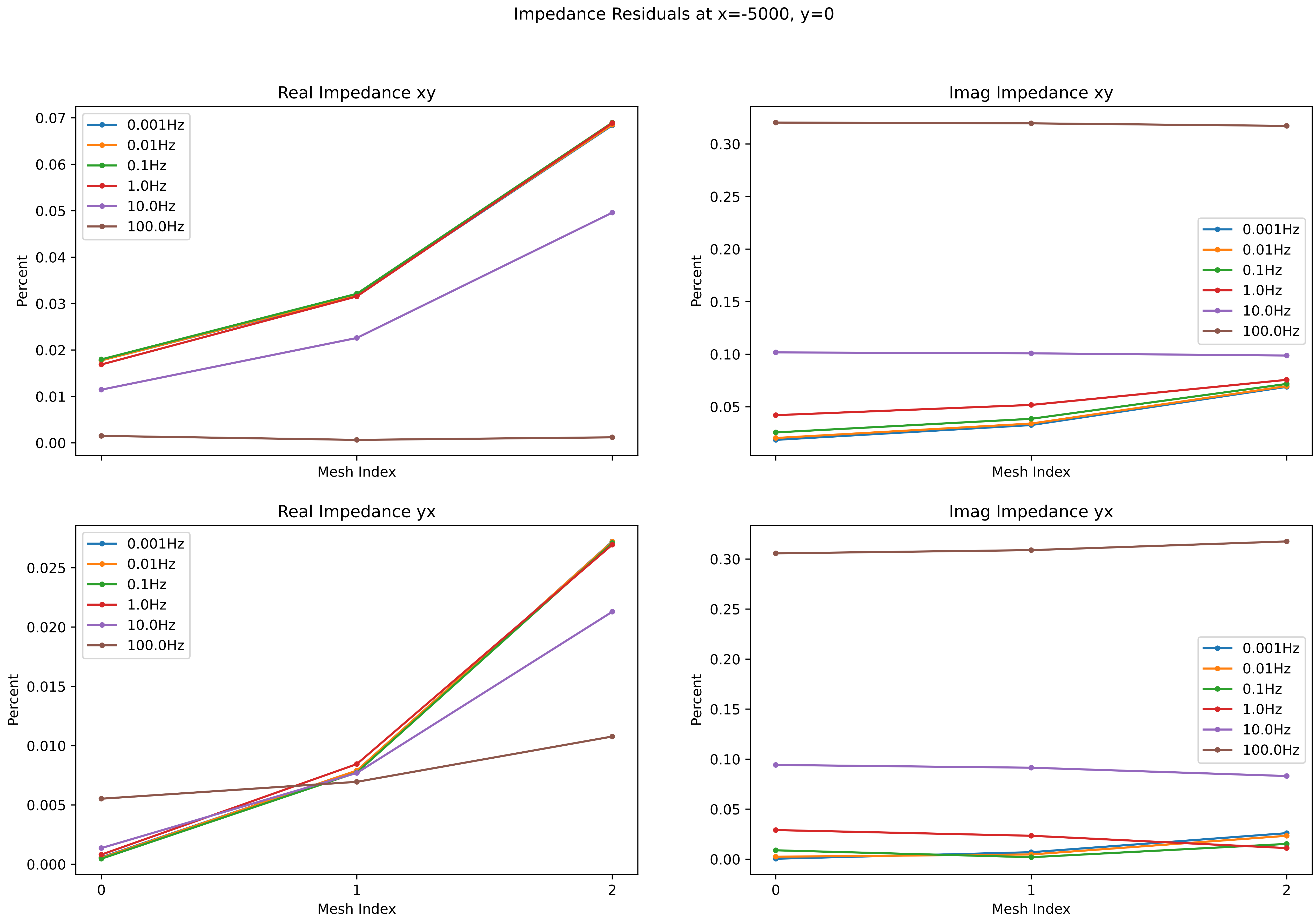
Impedance Residuals at x=-5000, y=0
Real Impedance xy
Imag Impedance xy
Real Impedance yx
Imag Impedance yx
Percent
Mesh Index
0.001Hz
0.01Hz
0.1Hz
1.0Hz
10.0Hz
100.0Hz
0.00
0.01
0.02
0.03
0.04
0.05
0.06
0.07
0.05
0.10
0.15
0.20
0.25
0.30
0.000
0.005
0.010
0.015
0.020
0.025
0
1
2

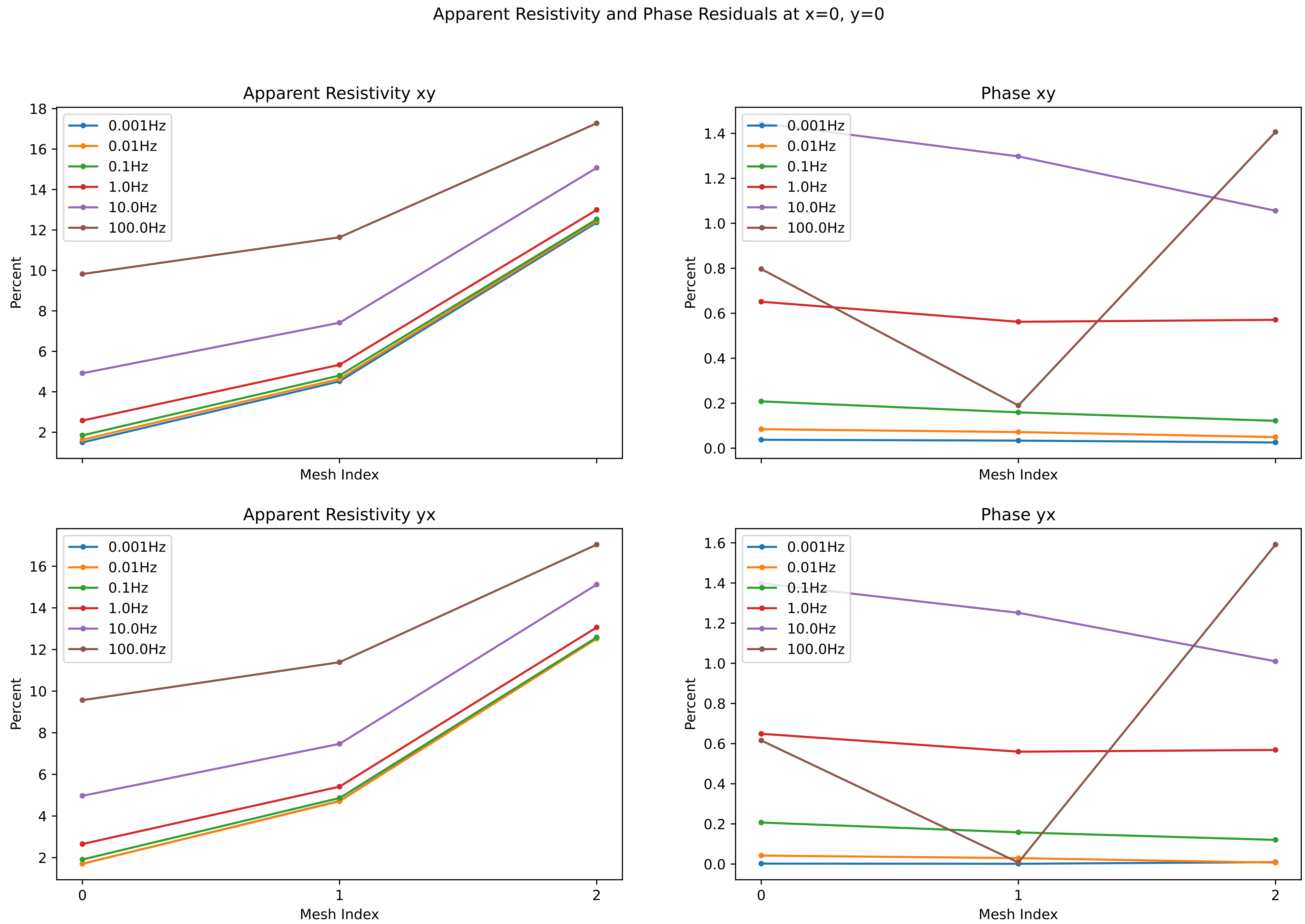

Apparent Resistivity and Phase Residuals at x=0, y=0
Apparent Resistivity xy
Phase xy
Apparent Resistivity yx
Phase yx
Percent
Mesh Index
0.001Hz
0.01Hz
0.1Hz
1.0Hz
10.0Hz
100.0Hz

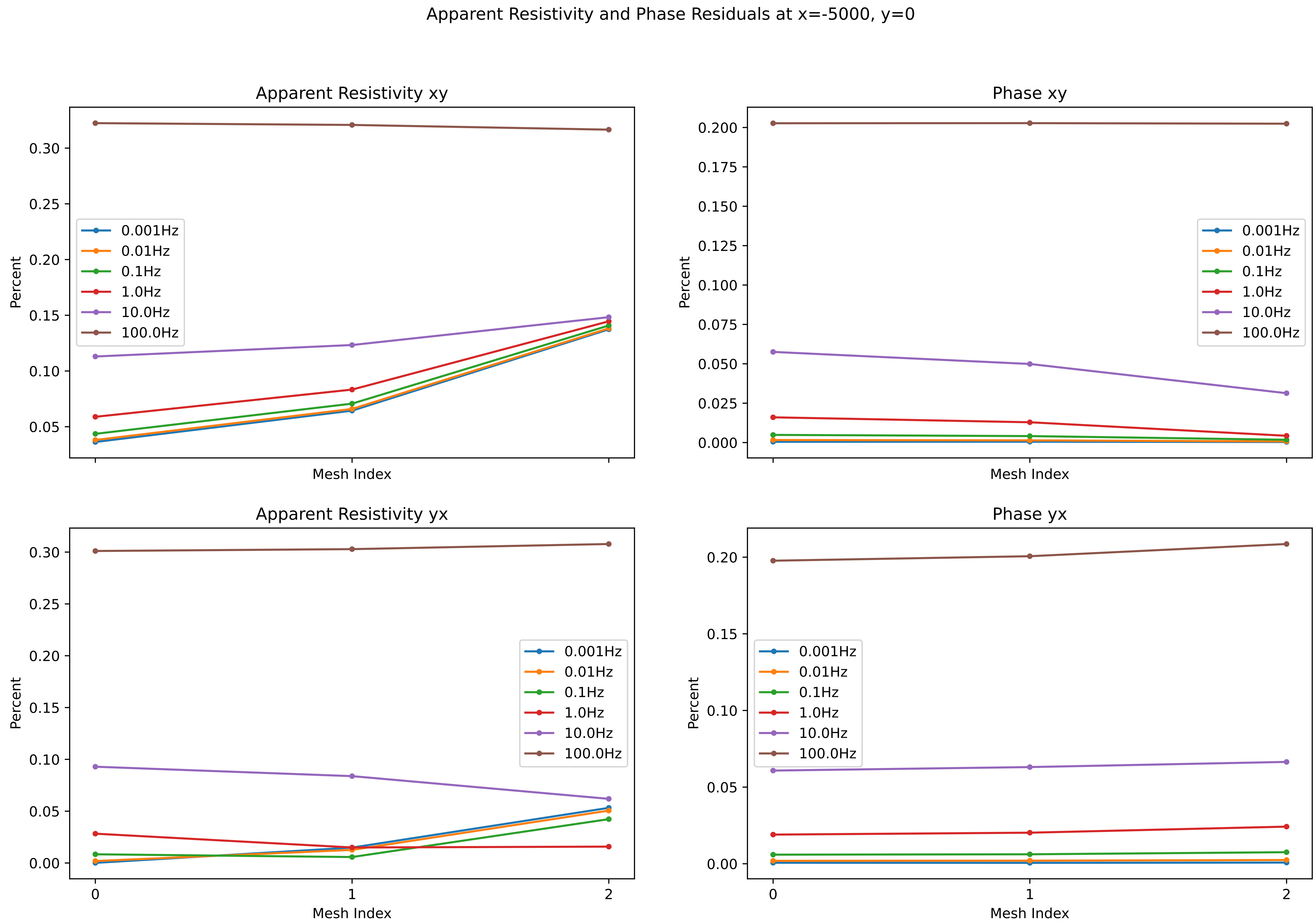
Apparent Resistivity and Phase Residuals at x=-5000, y=0
Apparent Resistivity xy
Phase xy
Apparent Resistivity yx
Phase yx
Percent
Mesh Index
0.001Hz
0.01Hz
0.1Hz
1.0Hz
10.0Hz
100.0Hz
0
1
2

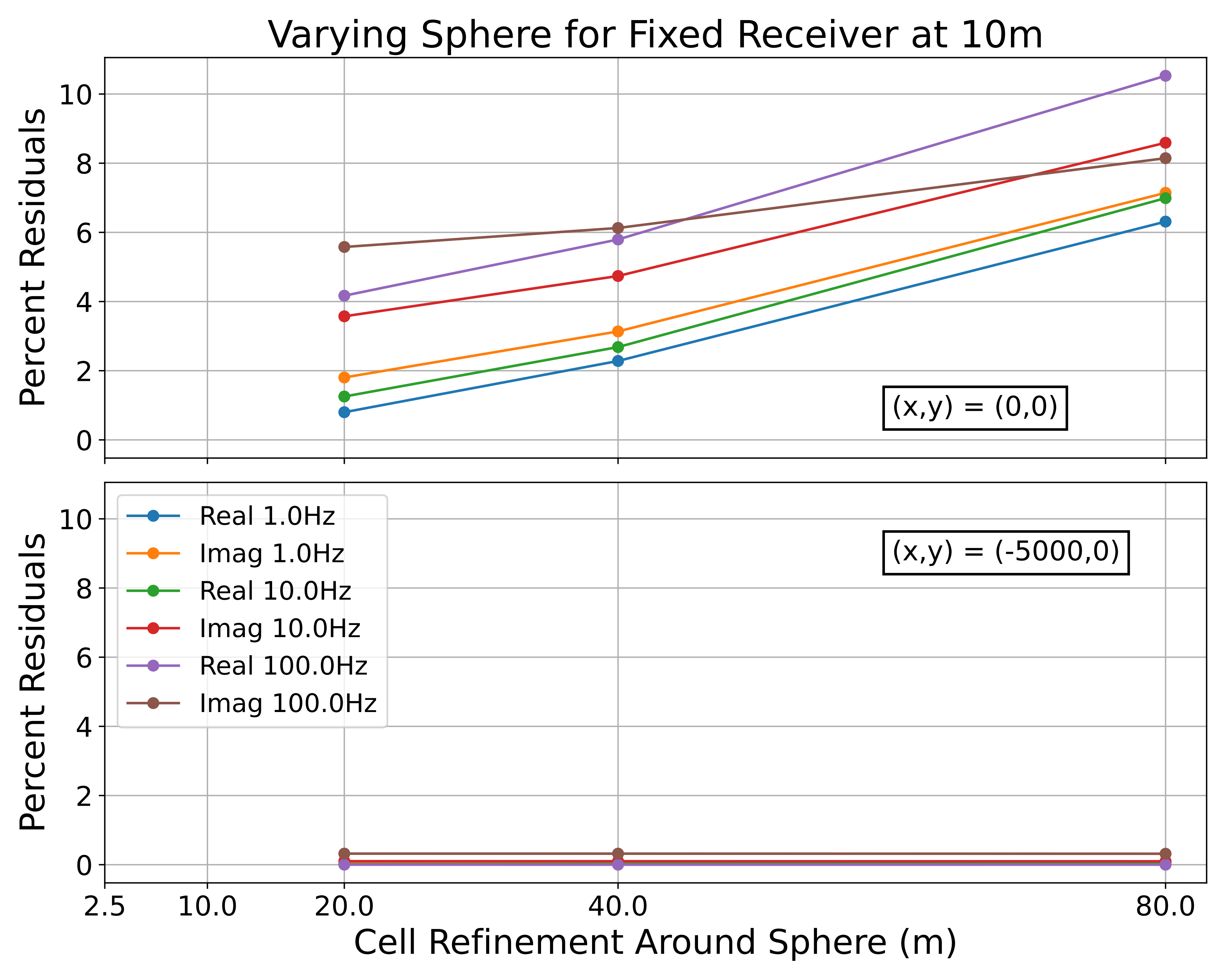

Varying Sphere for Fixed Receiver at 10m
Percent Residuals
(x,y) = (0,0)
(x,y) = (-5000,0)
Real 1.0Hz
Imag 1.0Hz
Real 10.0Hz
Imag 10.0Hz
Real 100.0Hz
Imag 100.0Hz
0
2
4
6
8
10
2.5
10.0
20.0
40.0
80.0
Cell Refinement Around Sphere (m)

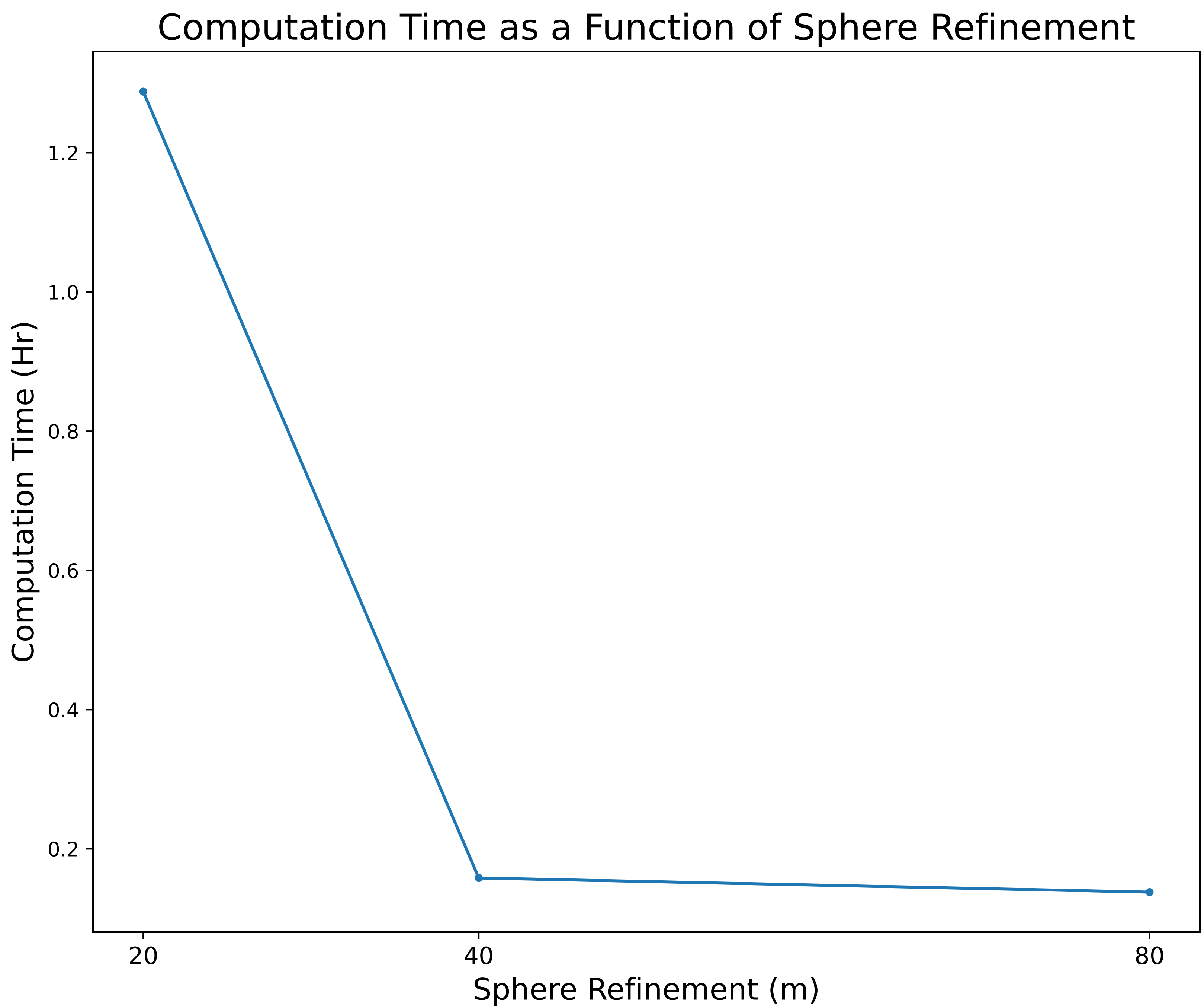
Computation Time as a Function of Sphere Refinement
Computation Time (Hr)
1.2
1.0
0.8
0.6
0.4
0.2
20
40
80
Sphere Refinement (m)